

## UE20CS206

**3<sup>rd</sup> Semester, Academic Year 2020-21**

Date:

Name:YAMAN GUPTA	SRN: PES2UG21CS619	Section J
------------------	-----------------------	--------------

Week#\_5\_\_\_\_\_

Program Number :\_1\_\_\_\_\_

Title

of the Program

### REGISTER FILE

Aim:

**AIM: TO CONSTRUCT A REGISTER FILE, FROM WHICH TWO 16-BIT VALUES CAN BE READ, AND TO WHICH ONE 16-BIT VALUE WRITTEN, EVERY CLOCK CYCLE.**

1: Paste the Screen Shot of the source code in reg\_alu.v

```

module dfrl_16 (input wire clk, reset, load, input wire [0:15] in, output wire [0:15] out);
    dfrl dfrl_0(clk, reset, load, in[0], out[0]);
    dfrl dfrl_1(clk, reset, load, in[1], out[1]);
    dfrl dfrl_2(clk, reset, load, in[2], out[2]);
    dfrl dfrl_3(clk, reset, load, in[3], out[3]);
    dfrl dfrl_4(clk, reset, load, in[4], out[4]);
    dfrl dfrl_5(clk, reset, load, in[5], out[5]);
    dfrl dfrl_6(clk, reset, load, in[6], out[6]);
    dfrl dfrl_7(clk, reset, load, in[7], out[7]);
    dfrl dfrl_8(clk, reset, load, in[8], out[8]);
    dfrl dfrl_9(clk, reset, load, in[9], out[9]);
    dfrl dfrl_10(clk, reset, load, in[10], out[10]);
    dfrl dfrl_11(clk, reset, load, in[11], out[11]);
    dfrl dfrl_12(clk, reset, load, in[12], out[12]);
    dfrl dfrl_13(clk, reset, load, in[13], out[13]);
    dfrl dfrl_14(clk, reset, load, in[14], out[14]);
    dfrl dfrl_15(clk, reset, load, in[15], out[15]);
endmodule

module mux2_16 (input wire [15:0] i0, i1, input wire j, output wire [15:0] o);
    mux2 mux2_0 (i0[0], i1[0], j, o[0]);
    mux2 mux2_1 (i0[1], i1[1], j, o[1]);
    mux2 mux2_2 (i0[2], i1[2], j, o[2]);
    mux2 mux2_3 (i0[3], i1[3], j, o[3]);
    mux2 mux2_4 (i0[4], i1[4], j, o[4]);
    mux2 mux2_5 (i0[5], i1[5], j, o[5]);
    mux2 mux2_6 (i0[6], i1[6], j, o[6]);
    mux2 mux2_7 (i0[7], i1[7], j, o[7]);
    mux2 mux2_8 (i0[8], i1[8], j, o[8]);
    mux2 mux2_9 (i0[9], i1[9], j, o[9]);
    mux2 mux2_10 (i0[10], i1[10], j, o[10]);
    mux2 mux2_11 (i0[11], i1[11], j, o[11]);
    mux2 mux2_12 (i0[12], i1[12], j, o[12]);
    mux2 mux2_13 (i0[13], i1[13], j, o[13]);
    mux2 mux2_14 (i0[14], i1[14], j, o[14]);
    mux2 mux2_15 (i0[15], i1[15], j, o[15]);
endmodule

module mux8_16 (input wire [0:15] i0, i1, i2, i3, i4, i5, i6, i7, input wire [0:2] j, output wire [0:15] o);
    mux8 mux8_0({i0[0], i1[0], i2[0], i3[0], i4[0], i5[0], i6[0], i7[0]}, j[0], j[1], j[2], o[0]);
    mux8 mux8_1({i0[1], i1[1], i2[1], i3[1], i4[1], i5[1], i6[1], i7[1]}, j[0], j[1], j[2], o[1]);
    mux8 mux8_2({i0[2], i1[2], i2[2], i3[2], i4[2], i5[2], i6[2], i7[2]}, j[0], j[1], j[2], o[2]);
    mux8 mux8_3({i0[3], i1[3], i2[3], i3[3], i4[3], i5[3], i6[3], i7[3]}, j[0], j[1], j[2], o[3]);
    mux8 mux8_4({i0[4], i1[4], i2[4], i3[4], i4[4], i5[4], i6[4], i7[4]}, j[0], j[1], j[2], o[4]);
    mux8 mux8_5({i0[5], i1[5], i2[5], i3[5], i4[5], i5[5], i6[5], i7[5]}, j[0], j[1], j[2], o[5]);
    mux8 mux8_6({i0[6], i1[6], i2[6], i3[6], i4[6], i5[6], i6[6], i7[6]}, j[0], j[1], j[2], o[6]);
    mux8 mux8_7({i0[7], i1[7], i2[7], i3[7], i4[7], i5[7], i6[7], i7[7]}, j[0], j[1], j[2], o[7]);
    mux8 mux8_8({i0[8], i1[8], i2[8], i3[8], i4[8], i5[8], i6[8], i7[8]}, j[0], j[1], j[2], o[8]);
    mux8 mux8_9({i0[9], i1[9], i2[9], i3[9], i4[9], i5[9], i6[9], i7[9]}, j[0], j[1], j[2], o[9]);
    mux8 mux8_10({i0[10], i1[10], i2[10], i3[10], i4[10], i5[10], i6[10], i7[10]}, j[0], j[1], j[2], o[10]);
    mux8 mux8_11({i0[11], i1[11], i2[11], i3[11], i4[11], i5[11], i6[11], i7[11]}, j[0], j[1], j[2], o[11]);
    mux8 mux8_12({i0[12], i1[12], i2[12], i3[12], i4[12], i5[12], i6[12], i7[12]}, j[0], j[1], j[2], o[12]);
    mux8 mux8_13({i0[13], i1[13], i2[13], i3[13], i4[13], i5[13], i6[13], i7[13]}, j[0], j[1], j[2], o[13]);
    mux8 mux8_14({i0[14], i1[14], i2[14], i3[14], i4[14], i5[14], i6[14], i7[14]}, j[0], j[1], j[2], o[14]);

```

```

mux8 mux8_14({i0[14], i1[14], i2[14], i3[14], i4[14], i5[14], i6[14], i7[14]}, j[0], j[1], j[2], o[14]);
mux8 mux8_15({i0[15], i1[15], i2[15], i3[15], i4[15], i5[15], i6[15], i7[15]}, j[0], j[1], j[2], o[15]);
endmodule

module reg_file (input wire clk, reset, wr, input wire [0:2] rd_addr_a, rd_addr_b, wr_addr, input wire [0:15] d_in, output wire [0:15] d_out_a, d_out_b);
  wire [0:7] load; wire [0:15] dout_0, dout_1, dout_2, dout_3, dout_4, dout_5, dout_6, dout_7;

  dfrl_16 dfrl_16_0(clk, reset, load[0], d_in, dout_0);
  dfrl_16 dfrl_16_1(clk, reset, load[1], d_in, dout_1);
  dfrl_16 dfrl_16_2(clk, reset, load[2], d_in, dout_2);
  dfrl_16 dfrl_16_3(clk, reset, load[3], d_in, dout_3);
  dfrl_16 dfrl_16_4(clk, reset, load[4], d_in, dout_4);
  dfrl_16 dfrl_16_5(clk, reset, load[5], d_in, dout_5);
  dfrl_16 dfrl_16_6(clk, reset, load[6], d_in, dout_6);
  dfrl_16 dfrl_16_7(clk, reset, load[7], d_in, dout_7);
  demux8 demux8_0(wr, wr_addr[2], wr_addr[1], wr_addr[0], load);
  mux8_16 mux8_16_0(dout_0, dout_1, dout_2, dout_3, dout_4, dout_5, dout_6, dout_7, rd_addr_a, d_out_a);
  mux8_16 mux8_16_10(dout_0, dout_1, dout_2, dout_3, dout_4, dout_5, dout_6, dout_7, rd_addr_b, d_out_b);
endmodule

module reg_alu (input wire clk, reset, sel, wr, input wire [1:0] op, input wire [2:0] rd_addr_a,
  rd_addr_b, wr_addr, input wire [15:0] d_in, output wire [15:0] d_out_a, d_out_b, output wire cout);
  wire [15:0] d_in_alu, d_in_reg; wire cout_0;
  alu alu_0(op, d_out_a, d_out_b, d_in_alu, cout_0);
  reg_file reg_file_0(clk, reset, wr, rd_addr_a, rd_addr_b, wr_addr, d_in_reg, d_out_a, d_out_b);
  mux2_16 mux2_16_0(d_in, d_in_alu, sel, d_in_reg);
  dfr dfr_0(clk, reset, cout_0, cout);
endmodule

```

## 2. Complete the truth table for all the 8 rows

sel	wr	op	rd_addr_a		rd_addr_b		wr_addr		d_in		Output	
28	27	26-25	24	23	22	21	20	19	1	17	16	Bit15 to Bit 0
									8			
0	1	xx	x	x	x	x	x	x	0	1	1	CDEF Reg3=CDEF
0	1	xx	x	x	x	x	x	x	1	1	1	3210 Reg7= 3210
0	1	xx	0	1	1	1	1	1	1	0	1	4567 Reg5=4567
0	1	xx	0	0	1	1	0	1	0	0	1	BA98 Reg1=BA98
0	0	xx	0	0	1	1	0	1	0	0	1	xxxx d_out_a=BA98 d_out_b=4567
1	1	00	0	0	1	1	0	1	0	1	0	xxxx Reg2=4567+BA98


=FFFF, cout =0



### **CASE2 (Write operation):**

sel =0,wr=1 ,Write Address=111,d\_in=3210,


Verify **in[15:0] of Register 7**

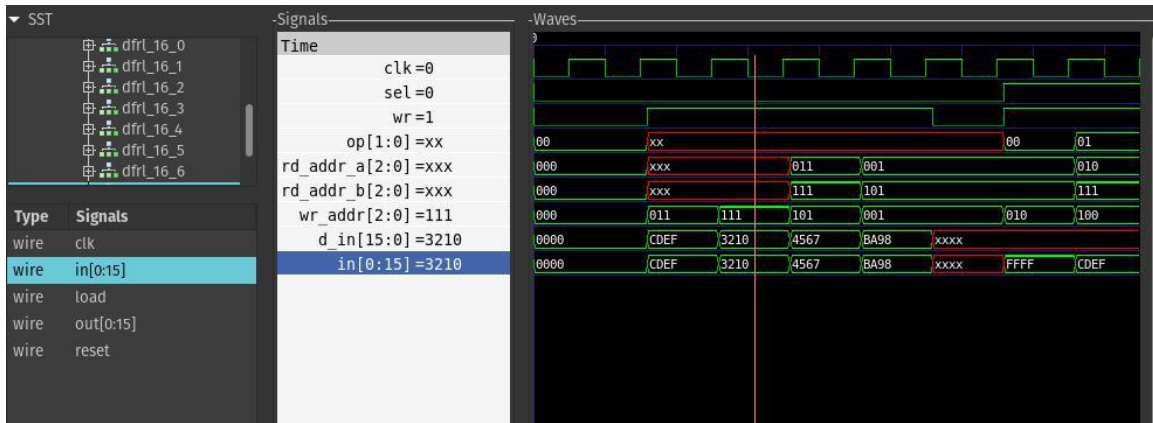

### III. SCREENSHOT 3

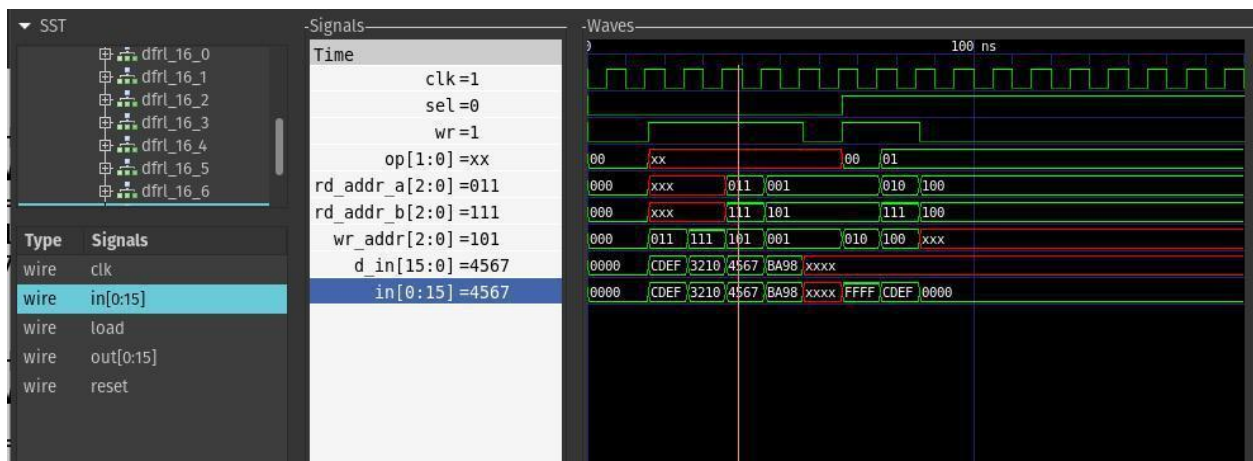
### CASE 3 (Write operation):

```
sel=0,wr=1 ,rd_addr_a=011, rd_addr_b=111,wr_addr=101,  
d_in=4567,Verify in[15:0] of Register 5
```



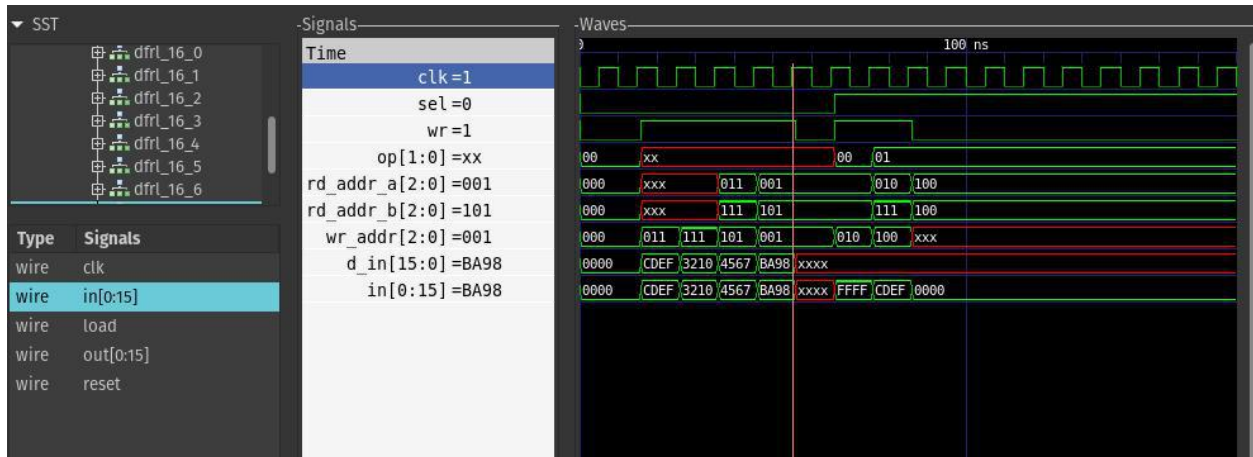
sel =0,wr=1 , rd\_addr\_a=001, rd\_addr\_b=101,wr\_addr=001,  
d\_in=BA98,Verify in[15:0] of Register 1





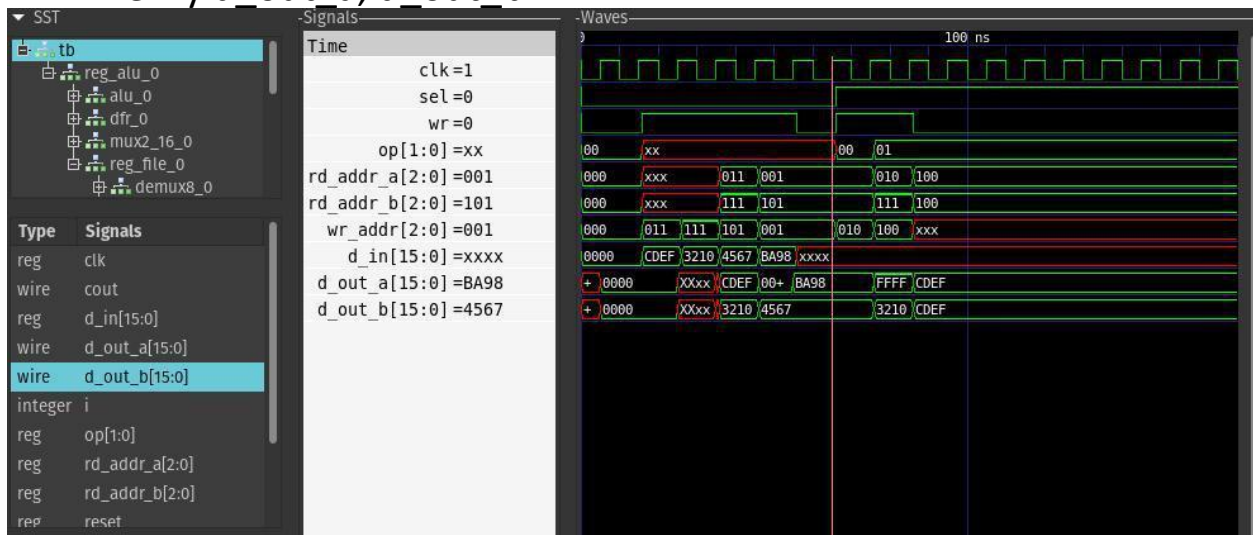
## V. SCREENSHOT 5 CASE 5 (Read operation):

sel=0,wr=0 , rd\_addr\_a=001, rd\_addr\_b=101,wr\_addr=001,  
Verify d\_out\_a, d\_out\_b



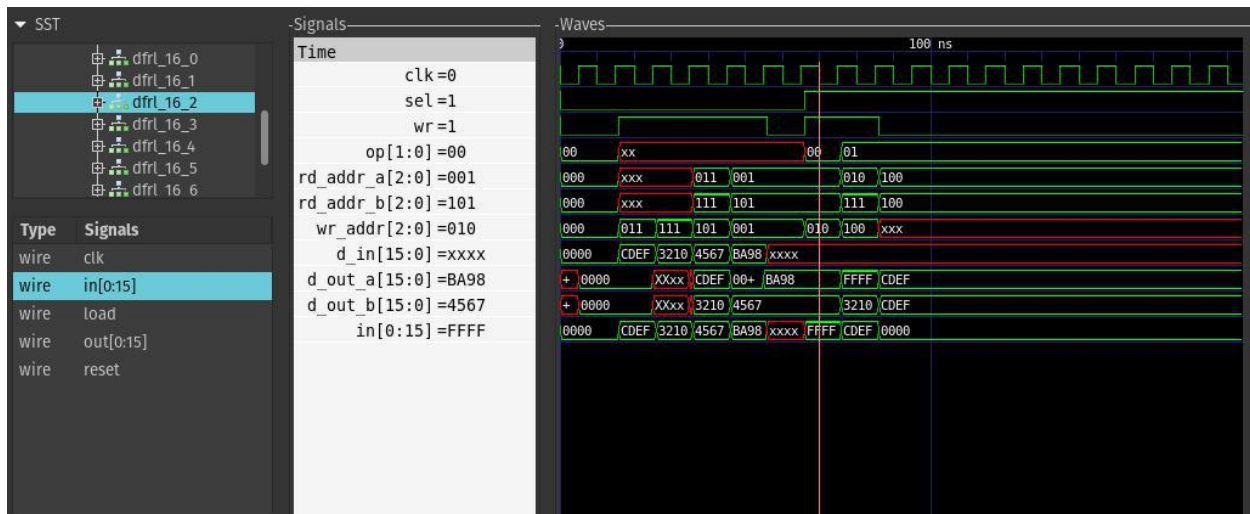
## VI. SCREENSHOT 6 CASE 6 (Write operation after addition):

sel =1,wr=1,op=00, rd\_addr\_a=001, rd\_addr\_b=101,wr\_addr=  
010 d\_in = XXXX,ALU output=d\_out\_a +  
d\_out\_b=4567+BA98=FFFF to be written to Reg2



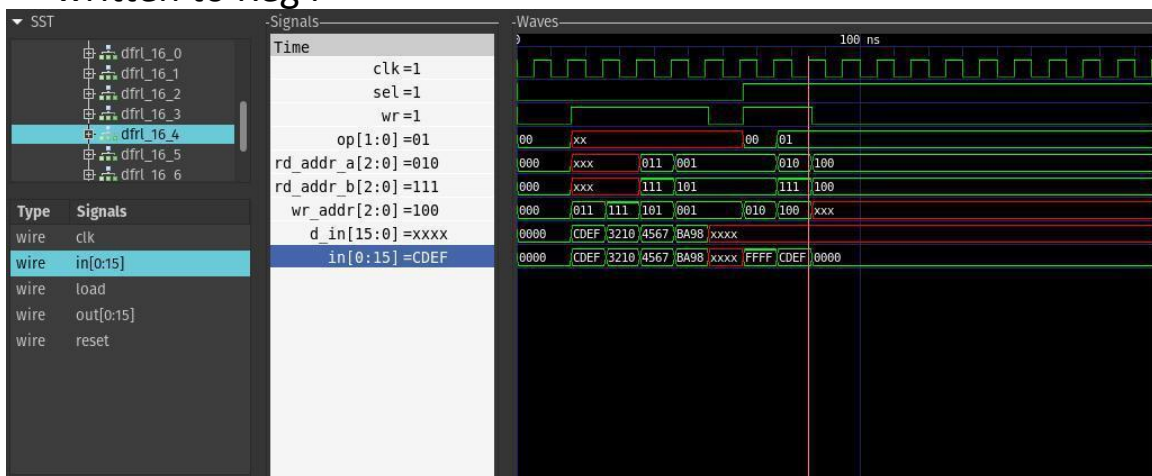
## VII. SCREENSHOT 7 CASE 7(Write operation after subtraction):

sel =1,wr=1,op=01, rd\_addr\_a=010, rd\_addr\_b=111,wr\_addr= 100  
d\_in = XXXX,ALU output=Reg2-Reg7=FFFF-3210=CDEF to be  
written to Reg4


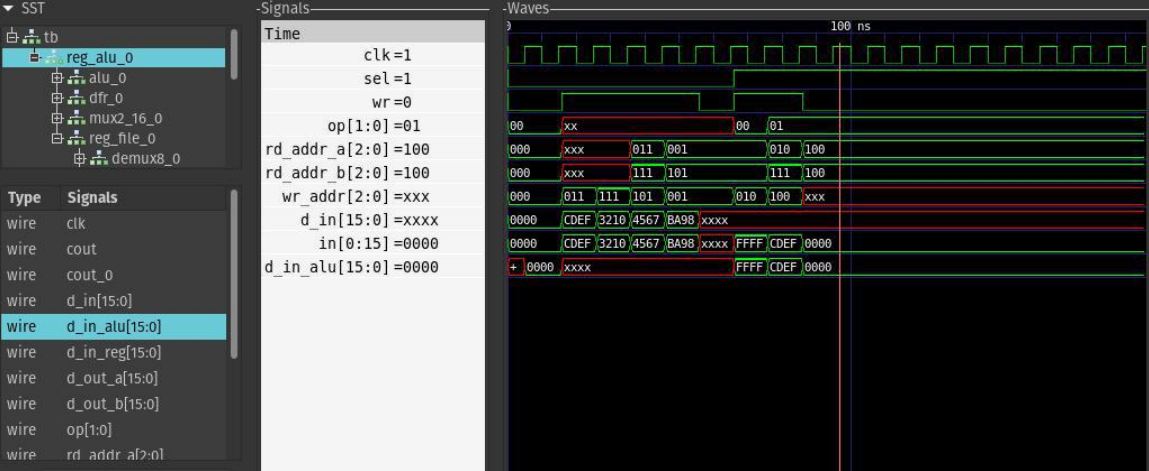
## VIII. SCREENSHOT 8 CASE 8(Write operation after subtraction):

sel =1,wr=0,op=01, rd\_addr\_a=100, rd\_addr\_b=100,wr\_addr= xxx  
d\_in = XXXX,ALU output=Reg4-Reg4=CDEF-CDEF =0000



### **Disclaimer:**

The programs and output submitted is duly written, verified and executed by me.

I have not copied from any of my peers nor from the external resource such as internet.

If found plagiarized, I will abide with the disciplinary action of the University.

Signature:YAMAN GUPTA

Name:YAMAN GUPTA

SRN: PES2UG21CS619

Section: J

Date: OCT 7TH,22