

Digital Design and Computer Organisation Laboratory

UE20CS256

3rd Semester, Academic Year 2021-22

Date: 24 August 2022

Name: yaman gupta	SRN: PES2UG21CS619	Section J
-------------------	---------------------------	------------------

Week# 1 Program Number: 1

TITLE:

WRITE A VERILOG PROGRAM TO MODEL A TWO INPUT AND GATE. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE AND GATE TRUTH TABLE

I. Verilog Code Screenshot

```
module andgate(a,b,y);  
input a,b;  
output y;  
assign y = a&b;  
endmodule
```


II. Verilog VVP Output Screen Shot

```

C:\iverilog\bin>vvp dsandgate.v
VCD info: dumpfile andout.vcd opened for output.
      0a=0, b=0, y=0
      5a=0, b=1, y=0
     15a=1, b=0, y=0
     30a=1, b=1, y=1


```

III. GTKWAVE Screenshot

 

IV. Output Table to be completed and included

2 - input AND gate

 

A	B	Output
0	0	0
0	1	0
1	0	0
1	1	1

Week#____1_____

Program Number:____2____

TITLE :

WRITE A VERILOG PROGRAM TO MODEL A TWO INPUT OR GATE. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE OR GATE TRUTH TABLE


I. Verilog Code Screenshot

```
module orgate(a,b,y);  
input a,b;  
output y;  
assign y = a|b;  
endmodule
```

ANSWER-

II.

Verilog VVP Output Screen Shot ANSWER-

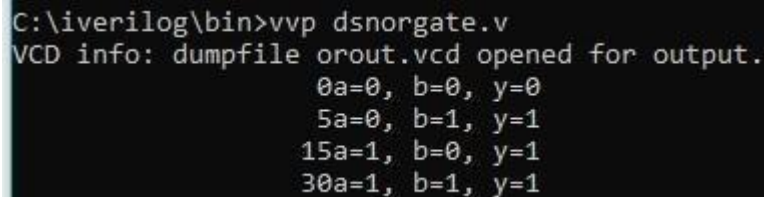


```
C:\iverilog\bin>vvp dsnorgate.v  
VCD info: dumpfile orout.vcd opened for output.  
0a=0, b=0, y=0  
5a=0, b=1, y=1  
15a=1, b=0, y=1  
30a=1, b=1, y=1
```

III. GTKWAVE


Screenshot

ANSWER-

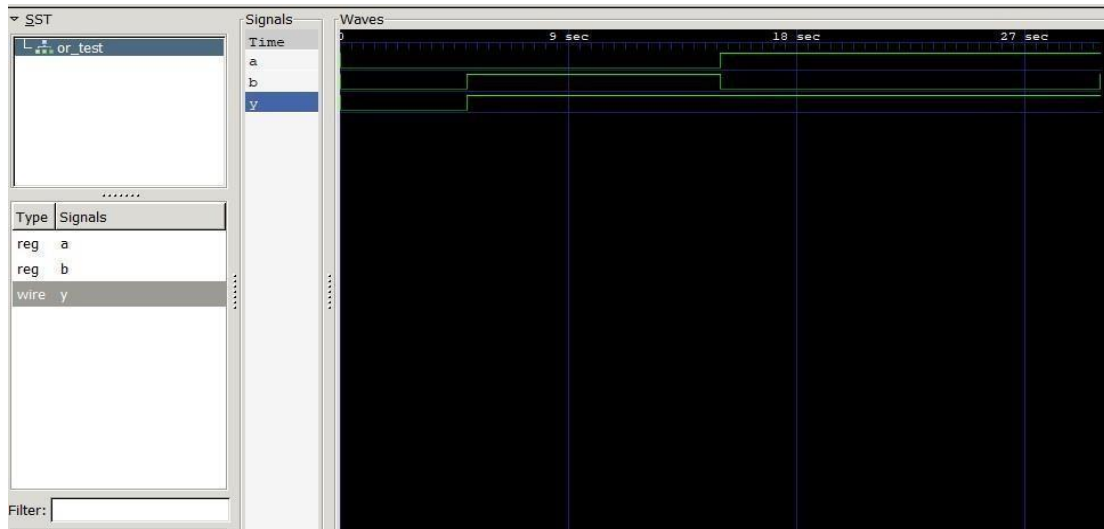

IV. Output Table to be completed and included

OR

 

Inputs		Output
A	B	C
0	0	0
0	1	1
1	0	1
1	1	1

Week# 1

Program Number:

3

TITLE:

WRITE A VERILOG PROGRAM TO MODEL A NOT GATE. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE NOT GATE TRUTH TABLE

I. Verilog Code Screenshot

```
module notgate(a,y);  
input a;  
output y;  
assign y = !a;  
endmodule
```

ANSWER-


II. Verilog VVP Output Screen Shot

```
C:\iverilog\bin>vvp dsnnnotgate.v  
VCD info: dumpfile notout.vcd opened for output.  
0a=0, y=1  
15a=1, y=0
```

ANSWER-


III. GTKWAVE Screenshot

Answer-

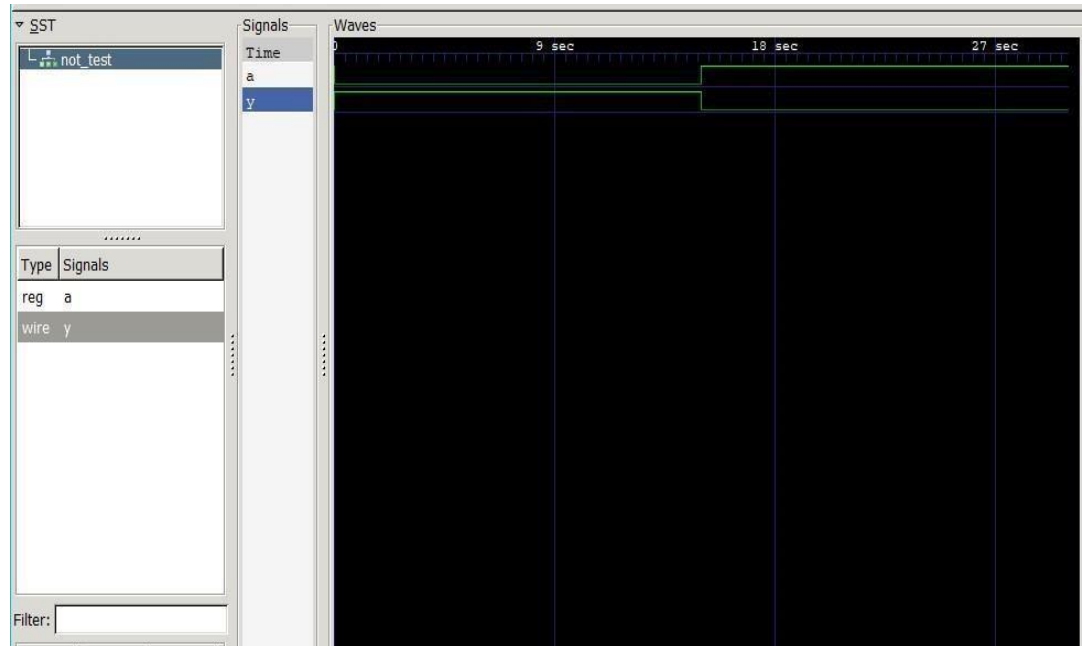

IV. Output Table to be completed and included

NOT Gate

 

Truth Table

INPUT	OUTPUT
A	NOT A
0	1
1	0

Week#____1_____ TITLE : Program Number:____4_____

WRITE A VERILOG PROGRAM TO MODEL A TWO INPUT NAND GATE. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE NAND GATE TRUTH TABLE

I. Verilog Code Screenshot

```
File Edit Format View Help
module nandgate(a,b,y);
input a,b;
output y;
assign y = a~&b;
endmodule
```

Answer-

II. Verilog VVP Output Screen Shot


```
C:\iverilog\bin>vvp dsnnandgate.v
VCD info: dumpfile nandout.vcd opened for output.
      0a=0, b=0, y=1
      5a=0, b=1, y=1
     15a=1, b=0, y=1
     30a=1, b=1, y=0
```

ANSWER-

III. GTKWAVE

Screenshot

ANSWER-

 

IV. Output Table to be completed and included



$$Q = A \text{ NAND } B$$

Truth Table

Input A	Input B	Output Q
0	0	1
0	1	1
1	0	1
1	1	0

Week# 1

Program Number:

5

TITLE:

WRITE A VERILOG PROGRAM TO MODEL A TWO INPUT NOR GATE. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE NOR GATE TRUTH TABLE

I. Verilog Code Screenshot

ANSWER-

```
module norgate(a,b,y);  
input a,b;  
output y;  
assign y = a~|b;  
endmodule
```

II.

Verilog VVP Output Screen Shot


ANSWER-

```
C:\iverilog\bin>vvp dsnnorgate.v  
VCD info: dumpfile norout.vcd opened for output.  
0a=0, b=0, y=1  
5a=0, b=1, y=0  
15a=1, b=0, y=0  
30a=1, b=1, y=0
```

III. GTKWAVE

Screenshot

ANSWER-

 

IV. Output Table to be completed and included

Input		Output
A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

Week#____1_____

Program Number:____6____TITLE:

**WRITE A VERILOG PROGRAM TO MODEL A TWO INPUT XOR GATE.
GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING
GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE AND GATE
TRUTH TABLE**

I. Verilog Code Screenshot

```
module xorgate(a,b,y);  
input a,b;  
output y;  
assign y = a^b;  
endmodule
```

ANSWER-


II.

Verilog VVP Output Screen Shot

```
C:\iverilog\bin>vvp dsnxorgate.v  
VCD info: dumpfile xorout.vcd opened for output.  
0a=0, b=0, y=0  
5a=0, b=1, y=1  
15a=1, b=0, y=1  
30a=1, b=1, y=0
```

ANSWER-

III. GTKWAVE Screenshot

 

ANSWER

IV Output Table to be completed and included

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

Week# 1

Program Number:

7

TITLE :

WRITE A VERILOG PROGRAM TO MODEL A TWO INPUT XNOR GATE. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE AND GATE TRUTH TABLE

I. Verilog Code Screenshot

```
FILE EDIT FORMATTING VIEW HELP
module xnorgate(a,b,y);
input a,b;
output y;
assign y = a~^b;
endmodule
```

ANSWER-


II. Verilog VVP Output Screen Shot

```
C:\iverilog\bin>vvp dsxnorgate.v
VCD info: dumpfile xnorout.vcd opened for output.
      0a=0, b=0, y=1
      5a=0, b=1, y=0
     15a=1, b=0, y=0
     30a=1, b=1, y=1
```


ANSWER-

III. GTKWAVE Screenshot

ANSWER-

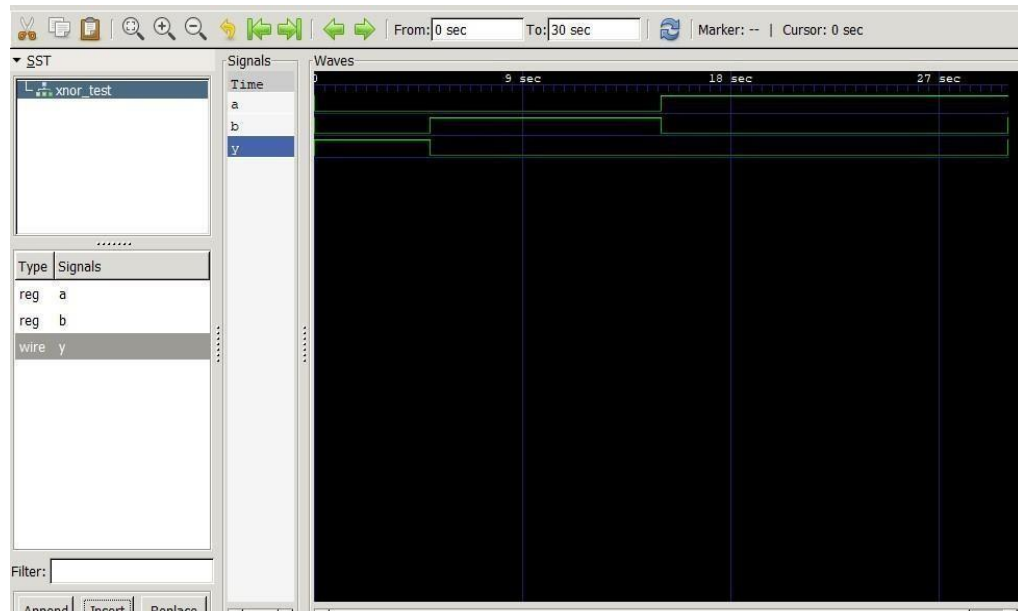

IV. Output Table to be completed and included

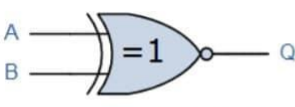Symbol	Truth Table		
 2-input Ex-NOR Gate	A	B	Q
	0	0	1
	0	1	0
	1	0	0
	1	1	1
Boolean Expression $Q = A \text{ XNOR } B$			

Disclaimer:

- The programs and output submitted is duly written, verified and executed by me.
- I have not copied from any of my peers nor from the external resource such as internet.
- If found plagiarized, I will abide with the disciplinary action of the University.

Signature:

Name: YAMAN GUPTA

SRN: PES2UG21CS619

Section: J

Date: 24 August 2022