

Digital Design and Computer Organization Laboratory

UE21CS251A

3rd Semester, Academic Year 2022-23

Date:

Name: YAMAN GUPTA	SRN:PES2UG21CS619	Section J
-------------------	-------------------	--------------


Week# ____2____

Program Number: ____1____

TITLE:

**WRITE A VERILOG PROGRAM TO MODEL A GIVEN LOGIC CIRCUIT.
GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING
GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE TRUTH
TABLE**

 
```
module simple_circuit(A,B,C,Y);  
  input A,B,C;  
  output Y;  
  wire X;  
  and G1(X,B,C);  
  or G2(Y,A,X);  
endmodule
```



I. Verilog Code Screenshot

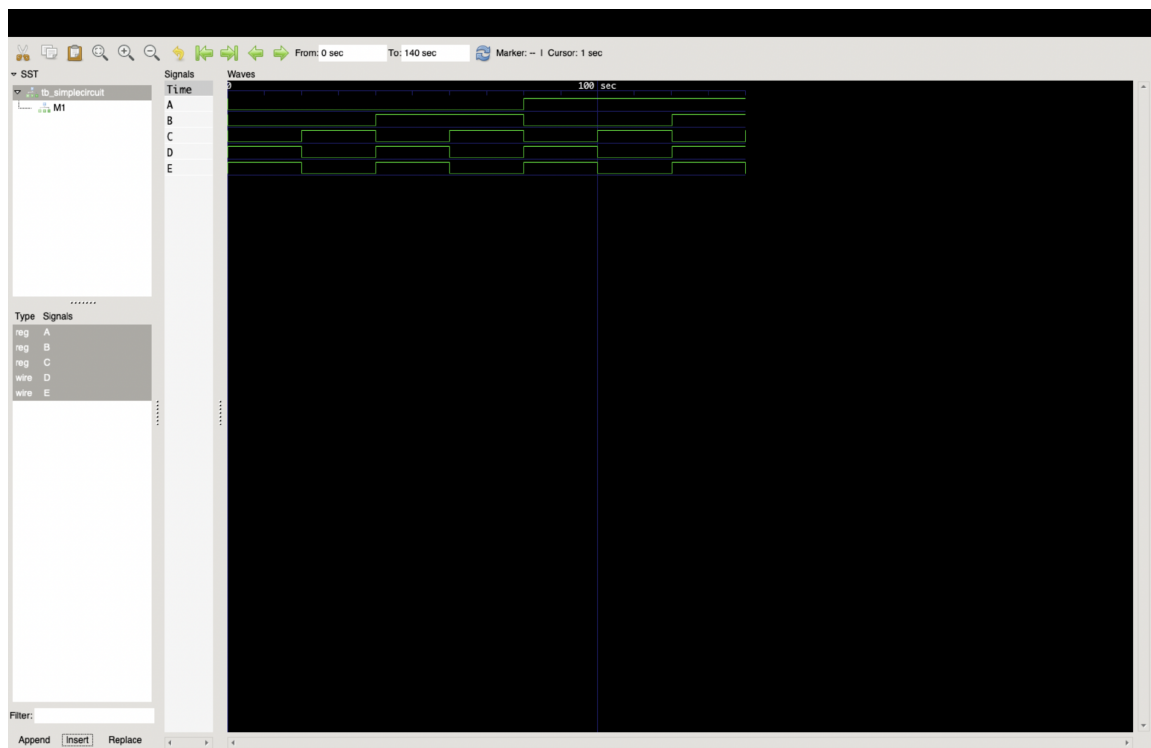II. Verilog VVP Output Screen Shot

```
Last login: Mon Aug 22 16:50:11 on console  
abhi@Abhisheks-MacBook-Pro ~ % cd desktop  
abhi@Abhisheks-MacBook-Pro desktop % cd ddcolab  
abhi@Abhisheks-MacBook-Pro ddcolab % iverilog -o tb_circuit1.v circuit1.v  
  
abhi@Abhisheks-MacBook-Pro ddcolab % vvp test  
  
VCD info: dumpfile simple.vcd opened for output.  
0A=0 B=0 C=0 D=1 E=1
```



III. GTKWAVE Screenshot

IV. Output Table to be completed and included


A	B	C	D	E
0	0	0	1	1
0	0	1	0	0
0	1	0	1	1
0	1	1	0	0
1	0	0	1	1
1	0	1	0	0
1	1	0	1	1
1	1	1	1	0

Week# ____1____

Program Number: ____2____

TITLE :

 WRITE A VERILOG PROGRAM TO MODEL A GIVEN LOGIC CIRCUIT. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE TRUTH TABLE




I. Verilog Code Screenshot

```
module simple_circuit(A2,B2,C2,Z);  
input A2,B2,C2;  
output Z;  
    wire Y1,Y2,Y3;  
    AND1: AND1(A2,B2,Y1);  
    AND2: AND2(B2,C2,Y2);  
    OR1: OR1(Y1,Y2,Y3);  
    OR2: OR2(Y2,Y3,Z);  
endmodule
```

```
abhi@Abhisheks-MacBook-Pro ddcolab % iverilog -o tb_circuit2.v circuit2.v
abhi@Abhisheks-MacBook-Pro ddcolab % vvp test
VCD info: dumpfile simple.vcd opened for output.
      0A=0,B=0,C=0,D=1,E=1
      20A=0,B=0,C=1,D=0,E=0
      40A=0,B=1,C=0,D=1,E=1
      60A=0,B=1,C=1,D=0,E=0
      80A=1,B=0,C=0,D=1,E=1
     100A=1,B=0,C=1,D=0,E=0
     120A=1,B=1,C=0,D=1,E=1
     140A=1,B=1,C=1,D=1,E=0
abhi@Abhisheks-MacBook-Pro ddcolab %
```

II. Verilog VVP Output Screen Shot

 

III. GTKWAVE Screenshot

IV. Output Table to be completed and included

A	B	C	D	E
0	0	0	1	1
0	0	1	0	1
0	1	0	1	1
0	1	1	0	0
1	0	0	1	0
1	0	1	0	0

1	1	0	1	0
1	1	1	1	0

Disclaimer:

- The programs and output submitted is duly written, verified and executed by me.
- I have not copied from any of my peers nor from the external resource such as internet.

- If found plagiarized, I will abide with the disciplinary action of the University.

Signature: YAMAN GUPTA

Name: YAMAN GUPTA

SRN: PES2UG21CS619

Date: 23/08/2022